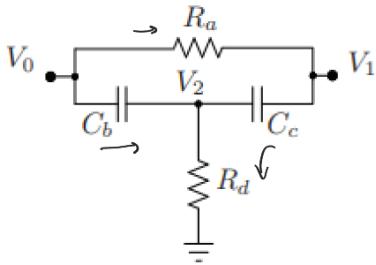


Q1: 1. Consider first the circuit shown at left in Figure 1, assuming that:

- (a) the voltage  $V_0(t)$  at the input node is specified precisely, regardless of the current  $I_0(t)$  drawn by the circuit, and
- (b) the current out the output node (if that node is connected to anything, to the right) is negligible,  $I_1(t) = 0$ .



1a. Write down the component equations across each of the 4 components, as well as KCL at the 3 "T" junctions (that is, at the left, at the right, and in the middle). Note that we have seven unknowns:  $\{V_1, V_2, I_0, I_a, I_b, I_c, I_d\}$ .

$$V_0 - V_1 = I_a R_a \dots (1), \quad I_o = I_a + I_b \dots (5)$$

$$I_a = I_c \dots (6)$$

$$I_d = I_b + I_c = I_o \text{ (dependent, not needed)} \dots (7)$$

$$C_b \frac{d(V_0 - V_2)}{dt} = I_b \dots (2)$$

$$C_c \frac{d(V_1 - V_2)}{dt} = I_c \dots (3)$$

$$V_2 - 0 = I_d R_d \dots (4)$$

1b. Take the Laplace transform of the 7 equations in question 1a, assuming zero initial conditions on all variables. Combine the 7 equations in 7 unknowns, by hand, to eliminate  $\{V_2, I_0, I_a, I_b, I_c, I_d\}$ , thereby developing a single equation for  $V_1(s)/V_0(s)$  in terms of the 4 parameters  $\{R_a, C_b, C_c, R_d\}$ .

$$(2) \xrightarrow{\mathcal{L}} C_b s (V_0 - V_2) = I_b \dots (1)$$

$$I_o = I_a + I_b = \sum_b + I_c = C_b s (V_0 - V_2) + C_c s (V_1 - V_2) \dots (2)$$

$$(3) \rightarrow C_c s (V_1 - V_2) = I_c \dots (3)$$

$$I_d = C_b s V_0 + C_c s V_1 - (C_b + C_c) s V_2 \dots (3)$$

$$\therefore V_1 - V_2 = \frac{1}{C_c s} I_c \dots (4)$$

$$\left( \frac{1}{R_d} + (C_b + C_c) s \right) V_2 \dots (4)$$

$$(2) \quad I_a = \frac{V_1}{R_a} = \frac{V_0 - V_1}{R_a} + C_b s (V_0 - V_2)$$

$$\left( \frac{1}{R_a} + C_b s \right) V_1 = \frac{V_0 - V_1}{R_a} + C_b V_0 s \quad \left( \frac{1}{R_a} + C_b s \right) \left( \frac{V_0 - V_1}{R_a} + C_b V_0 s \right) = (C_b V_0 + C_c V_1) s$$

$$\left( \frac{1}{R_a} + C_b s \right) V_2 = \frac{V_0 - V_1}{R_a} + C_b V_0 s \quad \left( \frac{1}{R_a} + C_b s \right) \left( \frac{1}{R_a} + C_c s \right) \left( \frac{1}{R_a} + C_b s \right) V_0 - \frac{1}{R_a} V_1 = C_b s V_0 + C_c s V_1$$

$$\frac{1 + (C_b + C_c) R_a s}{1 + C_b R_a s} \cdot \left( (1 + C_b R_a s) V_0 - V_1 \right) = C_b R_a s V_0 + C_c R_a s V_1$$

$$(1 + (C_b + C_c) R_d s) [(1 + C_b R_a s) V_0 - V_1] = (1 + C_b R_d s) [C_b R_a s V_0 + C_c R_a s V_1]$$

$$(1 + (C_b + C_c) R_d s) V_1 + (1 + C_b R_d s) C_c R_a s V_1 = + (1 + (C_b + C_c) R_d s) (1 + C_b R_a s) V_0 + (1 + C_b R_d s) C_b R_a s V_0$$

$$\frac{V_1}{V_0} = \frac{(1 + (C_b + C_c) R_d s) (1 + C_b R_a s) + (1 + C_b R_d s) C_b R_a s}{(1 + (C_b + C_c) R_d s) + (1 + C_b R_d s) C_c R_a s}$$

$$= \frac{1 - C_b R_a s + C_b^2 R_a R_d s^2 + C_b C_c R_a R_d s^2 + (C_b + C_c) R_d s + C_b R_a s + C_b^2 R_a R_d s^2}{1 + (C_b + C_c) R_d s + C_c R_a s + C_b C_c R_a R_d s^2}$$

$$\frac{V_1(s)}{V_0(s)} = \frac{C_b C_c R_a R_d s^2 + (C_b + C_c) R_d s + 1}{C_b C_c R_a R_d s^2 + [(C_b + C_c) R_d + C_c R_a] s + 1}$$


Quadratic formula:

$$m=2: \text{zeros } s = \frac{\omega}{2} (-1 \pm i\sqrt{3})$$

$$n=2: \text{poles } s = \frac{\omega}{2} (-3 \pm \sqrt{5})$$

for  $\omega = 10$ :

Bode Diagram

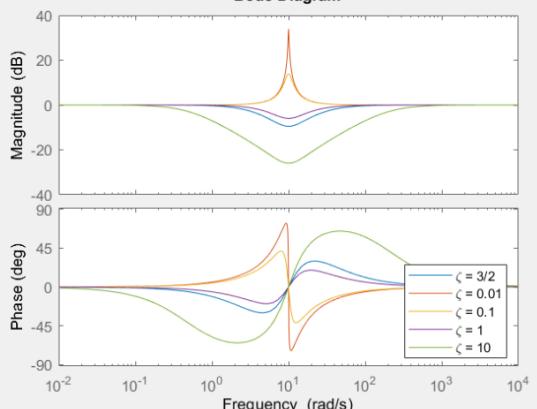

looking at how it rejects frequencies similar to the freq.  $\omega$  (so the tf lowers the gain of an input signal w/ freq. close to  $\omega$ ), it looks useful for filtering out noise near a given freq., or in a niche scenario, selectively amplifying it.

(d) turned everything in lab into matrix form (check code for further comments.)

Q 2. Repeat all four parts of question 1, in their entirety, for the circuit shown at right in Figure 1, subject to the same two assumptions.


→ means plug into

For question 2a, note that our seven unknowns are again denoted  $\{V_1, V_2, I_0, I_a, I_b, I_c, I_d\}$ .

For question 2b, develop a single equation for  $V_1(s)/V_0(s)$  in terms of the 4 new parameters  $\{C_a, R_b, R_c, C_d\}$ .

For question 2c, simplify by defining  $C_a = C/2$ ,  $R_b = R_c = R$ , and  $C_d = 2C$ , where  $R$  and  $C$  are kept as symbolics. 7

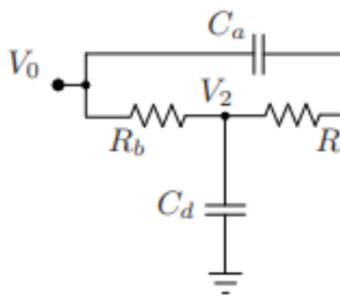For question 2d, now take  $\{s, V_0\}$  and  $\{C_a, R_b, R_c, C_d\}$  as symbolics.



2a & b)

$$(1) \dots I_0 = I_a + I_b$$

$$(2) \dots I_a = I_c$$

$$(3) \dots I_b + I_c = I_d = I_0$$

$$(4) \dots C_a \frac{d(V_0 - V_1)}{dt} = I_a = C_{as}(V_0 - V_1)$$

$$(5) \dots V_0 - V_2 = I_b R_b$$

$$(6) \dots V_1 - V_2 = I_c R_c$$

$$(7) \dots C_d \frac{d(V_2 - 0)}{dt} = I_d = C_{ds} V_2$$

$$C_{ds} V_2 = R_b^{-1}(V_0 - V_2) + R_c^{-1}(V_1 - V_2)$$

$$V_2(C_{ds} + R_b^{-1} + R_c^{-1}) = R_b^{-1}V_0 + R_c^{-1}V_1$$

$$(4, 6) \rightarrow 2$$

$$(V_1 - V_2)R_c^{-1} = C_{as}(V_0 - V_1)$$

$$V_2 = R_c C_{as}(V_1 - V_0) + V_1$$

$$[R_c C_{as}(V_1 - V_0) + V_1](C_{ds} + R_b^{-1} + R_c^{-1}) = R_b^{-1}V_0 + R_c^{-1}V_1$$

$$V_1 R_b^{-1} + V_1 R_c^{-1} - C_{as} V_0 s + C_{as} V_1 s + C_d V_1 s - C_a C_d R_c V_0 s^2 = R_b^{-1} V_0 + R_c^{-1} V_1 + C_a C_d R_c V_1 s^2 - C_a R_c R_b^{-1} V_0 s + C_a R_c R_b^{-1} V_1 s$$

$$V_1 [R_b^{-1} + s(C_a + C_d + C_a R_b^{-1} R_c) + s^2(C_a C_d R_c)] = V_0 [R_b^{-1} + s(C_a + C_a R_b^{-1} R_c) + s^2(C_a C_d R_c)]$$

$$V_1(s) = \frac{C_a C_d R_b R_c s^2 + C_a (R_b + R_c) s + 1}{C_a C_d R_b R_c s^2 + (C_a R_c + R_b (C_a + C_d)) s + 1},$$

$$C_a = C/2, C_d = 2C, R_b = R_c = R$$

$$2c) \frac{V_1(s)}{V_0(s)} = \frac{C^2 R^2 s^2 + C R s + 1}{C^2 R^2 s^2 + 3 C R s + 1} = \frac{s^2 + \frac{1}{CR} s + \frac{1}{C^2 R^2}}{s^2 + \frac{3}{CR} s + \frac{1}{C^2 R^2}}, \quad \omega = \frac{1}{CR}, \quad \frac{s^2 + \omega s + \omega^2}{s^2 + 3\omega s + \omega^2}, \quad 3\omega = 2\omega, \quad \zeta = 3/2$$

quadratic formula again.


$$\text{zeros: } s = \frac{\omega}{2} (-1 \pm i\sqrt{3})$$


$$\text{poles: } s = \frac{\omega}{2} (-3 \pm \sqrt{5})$$

everything mentioned in (1c) still applies, and the deciding factor between the two would most likely be size/geometry constraints.

2d) same as above... everything is commented on in the code.

Bode Diagram

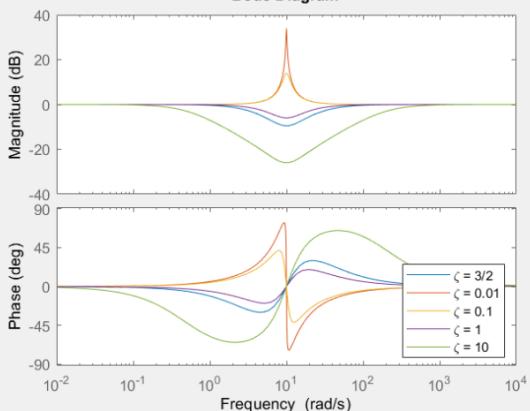

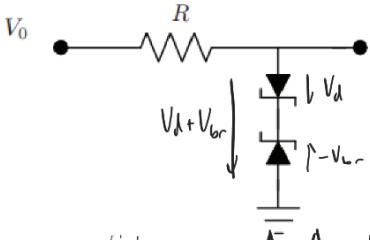

3. Consider a circuit with two zener diodes, attached "back-to-back" as illustrated at left in Figure 2. Assume both zener diodes have a breakdown voltage of  $V_{br} = 7.5$  V, a cut-in voltage of  $V_d = 0.7$  V, negligible leakage current, and a very steep  $I/V$  response outside the range  $V \in [-V_{br}, V_d]$ , as illustrated at right in Figure 2. Note that a zener diode is *not* a linear component, so we can *not* analyze a circuit like this with Laplace transforms and Bode plots. For the purpose of this exam, we will assume that  $V_0(t) = A \sin(\omega t)$ . We also assume, again, that:
- (a) the voltage  $V_0(t)$  at the input node is specified precisely, regardless of the current  $I_0(t)$  drawn by the circuit, and
  - (b) the current out of the output node (if that node is connected to anything, to the right) is negligible,  $I_1(t) = 0$ .

Figure 2: (left) The back-to-back zener filter considered in Problem 3, and (right) the current-voltage relationship of the zener diodes used, with  $V_{br} = 7.5$  V,  $V_d = 0.7$  V, and negligible leaking current.

- 3a. Subject to the assumptions listed above, if  $A$  is less than some threshold  $A_0$ , the output is the same as the input.  $V_1(t) = A \sin(\omega t)$ . Calculate  $A_0$ . What is the current through the Zener diodes in this case?


$$\text{as } A < A_0, \text{ the current through } R \text{ is } 0 \Rightarrow V_0 - V_1 = I R \Rightarrow V_1 = V_0 \\ = 0$$

$$, V_1 = A \sin(\omega t)$$

in the case of  $A < A_0$ ,  
here's no current flow through  
the zener diodes


in the case of  $A = A_0$ , the current is determined  
by  $I_R = I_z \rightarrow \frac{V_0}{R} = I_z$
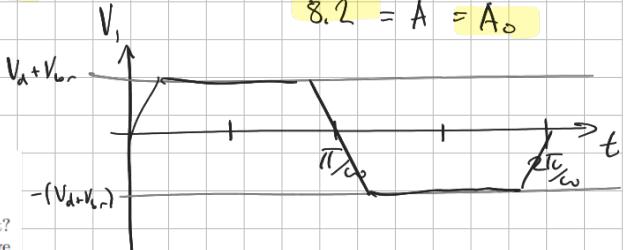
$$\text{at the peaks:} \\ V_1 = V_d + V_{br} = A \sin(\omega t) \\ 8.2 = A = A_0$$



- 3b. For  $A$  greater than the threshold  $A_0$  computed in question 3a, answer the following:

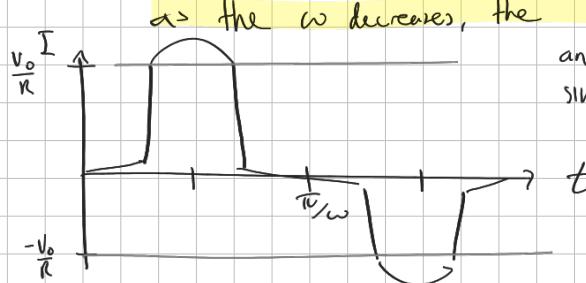- Plot  $V_1(t)$  in this case.
- Discuss how the shape of this output changes for different values of  $\omega$ .
- Plot the current through the Zener diodes, as a function of time, in this case. What is the value of the peak current?
- Discuss how to select  $R$ . Specifically, what would happen if we got rid of the resistor in this circuit (that is, if we took  $R \rightarrow 0$ )?



as the  $\omega$  decreases, the slope between each plateau is more gradual,  
and as  $\omega$  increases, the wave becomes more similar to a square wave.

$$\text{the } I_{\max} = \frac{V_0 \max}{R} = \frac{8.2}{R}$$

as  $R \rightarrow 0$ ,  $I_{\max} = \frac{V_0}{R} \rightarrow \infty$ ,  
which can damage the circuit  
and its elements.