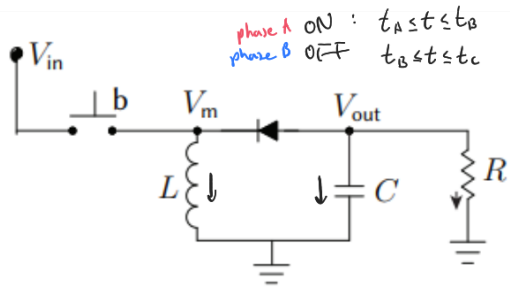


4 possible scenarios:



(1) ON Phase w/ no diode flow  
non zero  $I_C$ :  $f' = sF(s) - f(0)$   
 $V_m = V_i/s$   
 $V_m - 0 = L[sI_L - I_L^A]$   
 $I_C = C[sV_o - V_o^A]$   
 $V_o = I_R R$   
 $0 = I_C + I_R$

$$\left. \begin{aligned} V_o(s) &= \frac{CRV_o^A}{CRs + 1} \left( \frac{V_o^A}{s + 1/CR} \right) = \frac{V_o^A}{s + 1/CR} \\ I_L(s) &= (V_i + I_L^A Ls) / (Ls^2) \\ V_o(t) &= V_o^A e^{-(t-t_A)/CR} \\ I_L(t) &= I_L^A + V_i(t-t_A)/L \end{aligned} \right\} \text{IC's for next phase}$$

$$V_o^B = V_o(t_B) = V_o^A e^{-(t_B-t_A)/CR}$$

$$I_L^B = I_L(t_B) = I_L^A + V_i(t_B-t_A)/L$$

(2) ON phase w/ diode flow

$$V_o - V_m = V_d/s$$

$$V_m - 0 = L[sI_L - I_L^A]$$

$$I_C = C[sV_o - V_o^A]$$

$$-I_C - I_R = I_L$$

$$V_o = I_R R$$

$$\left. \begin{aligned} V_o(s) &= \frac{CLR V_o^A s^2 - LR I_L^A s + RV_d}{s(CLRs^2 + Ls + R)} \\ &= \frac{V_o^A s^2 - I_L^B C^{-1}s + C^{-1}L^{-1}V_d}{s(s^2 + C^{-1}R^{-1}s + C^{-1}L^{-1})} \\ &= \frac{b_2 s^2 + b_1 s + b_0}{s[s^2 + a_1 s + a_0]} \end{aligned} \right\}$$

$$\left. \begin{aligned} I_L(s) &= \frac{CLR I_L^A s^2 + (CR(V_o^A - V_d) + L I_L^A)s - V_d}{s(CLRs^2 + Ls + R)} \\ &= \frac{c_2 s^2 + c_1 s + c_0}{s[s^2 + a_1 s + a_0]} = \frac{'' + '' + ''}{s[(s+\sigma)^2 + \omega_d^2]} \\ &= \frac{C_2}{s} + C_1 \frac{s+\sigma}{(s+\sigma)^2 + \omega_d^2} + C_0 \frac{\omega_d}{(s+\sigma)^2 + \omega_d^2} \end{aligned} \right\}$$

$$b_2 = V_o^A, \quad a_1 = C^{-1}R^{-1}, \quad \sigma = a_1/2 = \frac{1}{2CR}, \quad c_2 = I_L^A$$

$$b_1 = -I_L^A/C, \quad a_0 = C^{-1}L^{-1}, \quad \omega_d = (a_0 - a_1^2/4)^{1/2}, \quad c_1 = I_L^A/CR + (V_o^A - V_d)/L$$

$$b_0 = V_d/(CLR), \quad \sigma = \frac{1}{2CR}, \quad c_0 = -V_d/(CLR)$$

following steps for  $\{B_2, B_1, B_0\}$ :

$$C_2 = -V_d/R$$

$$C_1 = I_L^A + V_d/R$$

$$C_0 = \frac{c_1 - c_2\sigma}{\omega_d} - C_2 \frac{\sigma}{\omega_d}$$

$$V_o(s) = \frac{B_2}{s} + B_1 \frac{s+\sigma}{(s+\sigma)^2 + \omega_d^2} + B_0 \frac{\omega_d}{(s+\sigma)^2 + \omega_d^2} \rightarrow V_o(t) = B_2 + B_1 e^{-\sigma(t-t_A)} \cos[\omega_d(t-t_A)]$$

$$B_2 = \lim_{s \rightarrow 0} s \left( \frac{b_2 s^2 + b_1 s + b_0}{s[s^2 + a_1 s + a_0]} \right) = \frac{b_0}{a_0} = V_d$$

$$B_1 = b_2 - B_2 = V_o^A - V_d$$

$$B_0 = \frac{b_1 - b_2\sigma}{\omega_d} - B_2 \frac{\sigma}{\omega_d} = -(I_L^A/C + V_o^A\sigma)/\omega_d - V_d \frac{\sigma}{\omega_d}$$

$$I_L(t) = C_2 + C_1 e^{-\sigma(t-t_A)} \cos[\omega_d(t-t_A)]$$

$$+ C_0 e^{-\sigma(t-t_A)} \sin[\omega_d(t-t_A)]$$

Find new IC's:  $V_o^B = V_o(t_B), I_L^B = I_L(t_B)$ 

(3) OFF phase w/o diode flow

$$V_m - 0 = L(sI_L - I_L^B)$$

$$I_C + I_R = 0 \quad \text{KCL @ } V_o \text{ node}$$

$$V_o = I_R R$$

$$-I_L = I_C + I_R$$

$$I_C = C(sV_o - V_o^B)$$

$$\left. \begin{aligned} V_o(s) &= \frac{CRV_o^B}{CRs + 1} = \frac{V_o^B}{s + 1/CR} \xrightarrow{\mathcal{L}^{-1}} V_o(t) = V_o^B e^{-(t-t_B)/CR} \\ I_L(s) &= 0 \rightarrow I_L(t) = 0 \\ V_o^C &= V_o(t_C) = V_o^B e^{-(t_C-t_B)/CR} \end{aligned} \right\} \text{for } t \in [t_B, t_C]$$

(4) OFF phase w/ diode flow

$$V_o - V_m = V_d/s$$

$$V_m - 0 = L(sI_L - I_L^B)$$

$$I_C = C(sV_o - V_o^B)$$

$$I_L = -I_R - I_C$$

$$V_o = I_R R$$

$$\left. \begin{aligned} V_o(s) &= \frac{CLR V_o^B s^2 - LR I_L^B s + RV_d}{s(CLRs^2 + Ls + R)} = \frac{V_o^B s^2 - I_L^B C^{-1}s + V_d C^{-1}L^{-1}}{s(s^2 + C^{-1}R^{-1}s + C^{-1}L^{-1})} = \frac{b_2 s^2 + b_1 s + b_0}{s[s^2 + a_1 s + a_0]} \\ I_L(s) &= \frac{CLR I_L^B s^2 + (CR(V_o^B - V_d) + L I_L^B)s - V_d}{s(CLRs^2 + Ls + R)} = \frac{c_2 s^2 + c_1 s + c_0}{s[s^2 + a_1 s + a_0]} \end{aligned} \right\}$$

We notice that the sys of eqn and thus our functions are equivalent to those in (2).

$$a_1 = C^{-1}R^{-1}$$

$$a_0 = C^{-1}L^{-1}$$

$$\sigma = a_1/2 = \frac{1}{2CR}$$

$$\omega_d = (a_0 - a_1^2/4)^{1/2}$$

$$= \left( \frac{1}{CR} - \frac{1}{4C^2R^2} \right)^{1/2}$$

$$b_2 = V_o^B, \quad c_2 = I_L^B$$

$$b_1 = -I_L^B/C, \quad c_1 = I_L^B/CR + (V_o^B - V_d)/L$$

$$b_0 = V_d/(CLR), \quad c_0 = -V_d/(CLR)$$

$$B_2 = V_d$$

$$B_1 = V_o^B - V_d$$

$$B_0 = \frac{b_1 - b_2\sigma}{\omega_d} - B_2 \frac{\sigma}{\omega_d} = \frac{I_L^B/C + V_o^B/(2CR)}{\left( \frac{1}{CL} - \frac{1}{4C^2R^2} \right)^{1/2}}$$

hence we get similar result w/ the PFE and  $\mathcal{L}^{-1}$ :

$$C_2 = -V_d/R$$

$$C_1 = I_L^B + V_d/R$$

$$C_0 = \frac{c_1 - c_2\sigma}{\omega_d} - C_2 \frac{\sigma}{\omega_d}$$

for  $t \in [t_B, t_C]$ 

$$V_o(t) = B_2 + B_1 e^{-\sigma(t-t_B)} \cos[\omega_d(t-t_B)]$$

$$+ B_2 e^{-\sigma(t-t_B)} \sin[\omega_d(t-t_B)]$$

$$I_L(t) = C_2 + C_1 e^{-\sigma(t-t_B)} \cos[\omega_d(t-t_B)]$$

$$+ C_2 e^{-\sigma(t-t_B)} \sin[\omega_d(t-t_B)]$$

scenarios (2) and (4) are when  $V_o > V_m + V_d$ ; when the  $V_o$  is able to overcome the cut-in voltage to have current thru the diode

for (1), current flows through  $V_{in}$  to gnd only through the L, and C and R are in series, driven by the discharge of the capacitor.  $I_L$  increases over time (so we can't just leave the  $V_{in}$  on or else it breaks) the  $V_o^B$  and  $I_L^B$  carry on to either OFF phase (3 or 4).

for (2), current flows through the L from both the diode and  $V_{in}$  into gnd, and from C and R into the diode. this would occur w/ sufficient charge built up in the C such that  $V_o^A > V_m + V_d$ . the  $V_o^B$  and  $I_L^B$  carry on to either OFF phase (3 or 4).

for (3), the setup is almost identical to (1), w/ R and C in series, and the L being isolated. however, the difference is that  $V_{in}$  is no longer connected, resulting in the  $I_L$  starting to decrease (but not instant since magnetic field)

for (4), the setup is almost identical to (2), w/ current flowing from R and C into the diode, and the inductor maintaining a current that flows into ground.

$I_L$  remains (+) and lags the voltage drop and its field induces a  $\Delta V$  in response to the  $\frac{dI}{dt}$  being (-), in turn  $\Delta(0 - V_m)$  is (-)  $\therefore V_m$  being (-), and  $V_{out} = 0$  puts the diode in fwd bias and lets current flow through assumption for (4).

As a result, the capacitor accumulates (+) charge on the gnd terminal, and its voltage drop  $\Delta(0 - V_{out})$  increases in magnitude

for periodic analysis where we reach a stabilized  $V_o$ ,  $V_o^A = V_o^C$  and  $I_L^A = I_L^C$  We can solve by using  $V_o(t_A) = V_o(t_C)$  w/ the functions and inputs: evaluate the following  
 $I_L(t_A) = I_L(t_C)$   
 $pA = t_B - t_A = f^{-1}D$   $V_o^B(pA, V_o^A), V_o^C(pB, V_o^B)$   $V_o^C(pB, V_o^B(pA, V_o^A)) = V_o^A$   
 $pB = t_C - t_B = (1-D)/f$   $I_L^B(pA, I_L^A), I_L^C(pB, I_L^B)$   $I_L^C(pB, I_L^B(pA, I_L^A)) = I_L^A$

$V_o^A = B_2 + e^{-\sigma pB} [B_1 \cos \omega pB + B_0 \sin \omega pB]$ , w/  $B_1, B_0, C_1, C_0$  needing  $V_o^B(pA, V_o^A)$  &  $I_L^B(pA, I_L^A)$  simplified  
 $I_L^A = C_2 + e^{-\sigma pB} [C_1 \cos \omega pB + C_0 \sin \omega pB]$  and then isolating  $V_o^A$  &  $I_L^A$  for a sys of 2 eqn and 2 unknown.

the on and off phases are a decaying exponential or sinusoid, and a higher duty cycle lets more charge accumulate on the C and gives more time for a stronger magnetic field to form from L, resulting in behavior like a boost converter.