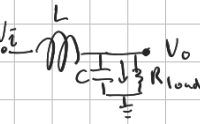


1) 

$$I_L = I_C + I_R, \quad I_L - I_C - I_R = 0$$

$$L \frac{dI_L}{dt} = V_i - V_o, \quad LsI_L + V_o = V_i$$

$$I_C = C \frac{dV_o}{dt}, \quad CsV_o - I_C = 0$$


$$V_o - 0 = I_R R_{load}, \quad I_R R_{load} - V_o = 0$$

$$\begin{pmatrix} 1 & -1 & -1 & 0 \\ Ls & 0 & 0 & 1 \\ 0 & -1 & 0 & Cs \\ 0 & 0 & R_{load} & -1 \end{pmatrix} \begin{pmatrix} I_L \\ I_C \\ I_R \\ V_o \end{pmatrix} = \begin{pmatrix} 0 \\ V_i \\ 0 \\ 0 \end{pmatrix}$$

$$X = A \backslash b$$

$$\text{solving for } V_o \text{ as a function of } V_i, X(4)$$

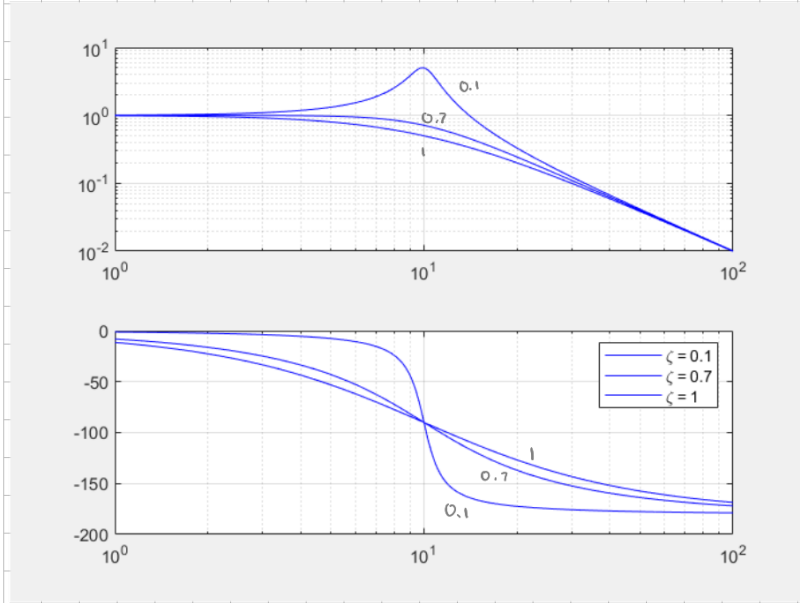2)
$$\frac{V_o(s)}{V_i(s)} = \frac{R_{load} / (R_{load} CL)}{s^2 + \frac{L}{R_{load} CL} s + \frac{R_{load}}{R_{load} CL}} = \frac{1/CL}{s^2 + \frac{1}{RC} s + \frac{1}{CL}} = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$




$\omega_n^2 = 1/CL \rightarrow \omega_n = 1/\sqrt{CL}$

$2\zeta\omega_n = \frac{1}{RC} \rightarrow \zeta = \frac{1}{2RC} \frac{(CL)^{1/2}}{1} = \frac{1}{2} L^{1/2} R_{load}^{-1} C^{-1/2} = \frac{1}{2R_{load}} \sqrt{L/C}$

the ζ value acts like a damping coeff., with smaller values increasing the degree of "resonance" of the system near certain frequencies.

(degree in a figurative sense, not mathematically)

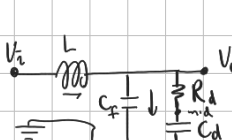3) 

$$I_L = I_{Cf} + I_{Rd}, \quad I_L - I_{Cf} - I_{Rd} = 0$$

$$I_{Cd} = I_{Ra}, \quad I_{Rd} - I_{Cd} = 0$$

$$L \frac{dI_L}{dt} = V_i - V_o, \quad LsI_L + V_o = V_i$$

$$C_f \frac{d(V_o - 0)}{dt} = I_{Cf}, \quad -I_{Cf} + C_f s V_o = 0$$

$$I_{Rd} R_d = V_o - V_{mid}, \quad R_d I_{Rd} - V_o + V_{mid} = 0$$

$$C_d \frac{d(V_{mid} - 0)}{dt} = I_{Cd}, \quad -I_{Cd} + C_d s V_{mid} = 0$$

$$\begin{pmatrix} 1 & -1 & -1 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 & 0 \\ Ls & 0 & 0 & 0 & 1 & 0 \\ 0 & -1 & 0 & 0 & C_f s & 0 \\ 0 & 0 & 0 & R_d & -1 & 1 \\ 0 & 0 & -1 & 0 & 0 & C_d s \end{pmatrix} \begin{pmatrix} I_L \\ I_{Cf} \\ I_{Cd} \\ I_{Rd} \\ V_o \\ V_{mid} \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ V_i \\ 0 \\ 0 \\ 0 \end{pmatrix}$$

$$V_o = \frac{C_d R_d s + 1}{C_d C_f L R_d s^3 + (C_d + C_f) L s^2 + C_d R_d s + 1} V_i$$

$$\frac{V_o(s)}{V_i(s)} = \frac{C_d R_d s + 1}{C_d C_f L R_d s^3 + (C_d + C_f) L s^2 + C_d R_d s + 1} = \frac{s + (C_d R_d)^{-1}}{C_f L s^3 + \left(\frac{C_d + C_f}{C_d R_d}\right) L s^2 + s + (C_d R_d)^{-1}} = \frac{s + \omega}{C_f L s^3 + L \omega (C_d + C_f) s^2 + s + \omega}$$

$$\omega = \frac{1}{C_d R_d}$$

```
F_PDF =
RR_tf with properties:
num:[1/(Cf*L), 1/(4*Cf^2*L*(L/Cf)^(1/2))]
den:[1, 5/(4*Cf*(L/Cf)^(1/2)), 1/(Cf*L), 1/(4*Cf^2*L*(L/Cf)^(1/2))]
Continuous-time transfer function
m=1, n=3, n_r=n-m=2, strictly proper, K=1/(Cf*L)
z:-1/(4*Cf*(L/Cf)^(1/2))
p:[((12*87^(1/2)*Cf^3*(L/Cf)^(3/2)*(1/(Cf^3*L^3))^(1/2) + 19)/(Cf^3*(L/Cf)^(1/2)))]
>> F_undamped
F_undamped =
RR_tf with properties:
num: 100
den: 1 20 100
Continuous-time transfer function
m=0, n=2, n_r=n-m=2, strictly proper, K= 100
z: p: -10 -10
```

we can see that the modified circuit now has 1 zero and 3 poles, compared to the previous which had no zeros and 2 poles. this still gives us a strictly proper transfer function.

$$4) \quad R_d = \sqrt{L/C_f}, \quad C_d = 4C_f \quad \rightarrow \quad \omega = \frac{1}{C_d R_d} = \frac{1}{4C_f \sqrt{L/C_f}} = \frac{1}{4C_f^{1/2} L^{1/2}} = \frac{1}{4\sqrt{C_f L}}$$


$$\frac{V_o(s)}{V_i(s)} = \frac{s + \omega}{C_f L s^3 + L\omega(C_d + C_f)s^2 + s + \omega} = \frac{s + \omega}{C_f L s^3 + 5C_f L \omega s^2 + s + \omega}$$

$$\text{tot: } \omega = 10 = 1/4\sqrt{C_f L} \quad \rightarrow \quad C_f L = \frac{1}{40^2} \quad \rightarrow \quad \frac{V_o(s)}{V_i(s)} = \frac{s + 10}{\frac{1}{1600} s^3 + \frac{5}{160} s^2 + s + 10}$$

```

F_PDF_2 =
RR_tf with properties:
num:      1600      16000
den:      1          50          1600          16000
Continuous-time transfer function
m=1, n=3, n_r=n-m=2, strictly proper, K=      1600
z:      -10
p:      -14.8389 + 0.0000i -17.5806 -27.7340i -17.5806 +27.7340i

```

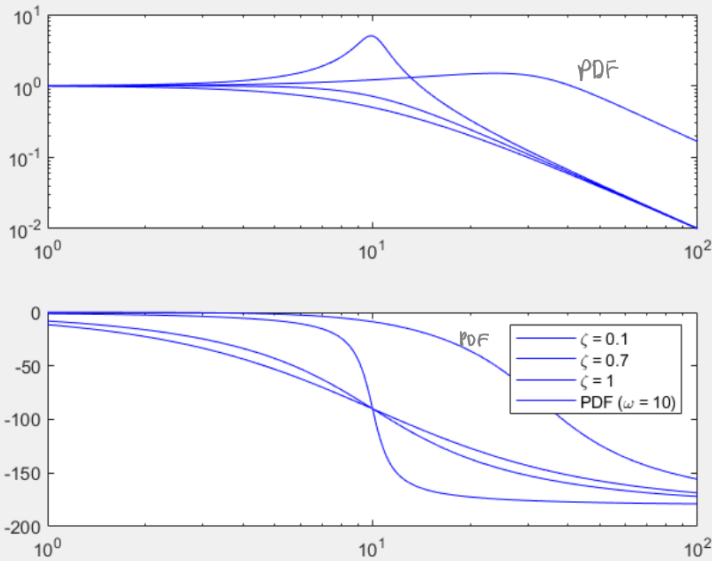

we can observe that for the same frequency $\omega = 10$, the response is more subdued, which can be attributed to larger poles (toward LHP), and as a consequence, the breakpoint has shifted further right, and while there's a complex conjugate pair, its effects are not as noticeable because of how close it is to the other breakpoint.

The " $5C_f L \omega s^2$ " term in the denominator behaves similarly to s , as reducing its value makes the complex conj. pair have a greater presence in the plot.